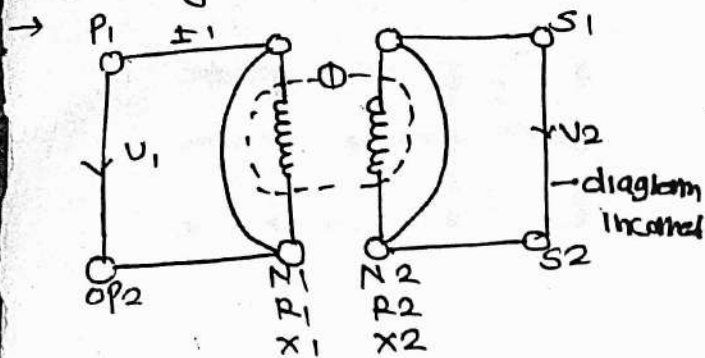


2) Derive the emf equation of single-phase transformer




From figure mathematical equation of Flux (ϕ) given by

$$\phi = \phi_m \sin \omega t$$

As we know that.

$$\omega = 2\pi f$$
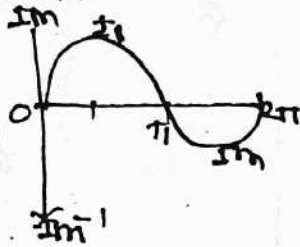
$$\therefore \phi = \phi_m \sin 2\pi f t$$



$$e = -N \frac{d\phi}{dt} \quad N - \text{no. of turn coil}$$

ϕ - Rate of change Flux

$$e = -N \frac{d\phi}{dt} (\phi_m \sin 2\pi f t)$$

$$e = -N \phi_m \frac{d}{dt} (\sin 2\pi f t)$$

$$e = -N \phi_m \cos(2\pi f t) \cdot 2\pi f$$

Now $\cos(2\pi f t) = \pm 1$

$$\therefore e_{\max} = -N \phi_m 2\pi f (\pm 1)$$

$$\therefore e_{\max} = N \phi_m \cdot 2\pi f$$

$$E_{\text{rms}} = \frac{e_{\max}}{\sqrt{2}} = 4.44 \cdot N \phi_m f$$


Primary induced emf

$$E_1 = 4.44 N_1 \phi_m f$$

$$E_2 = 4.44 N_2 \phi_m f$$

Single phase
Transformer

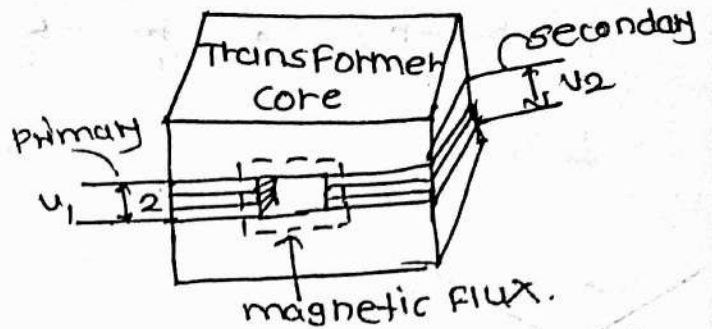Derive the expression for the transformer for delta connection



Turn ratio of transformation

$$\therefore \text{Turn ratio} = \frac{N_1}{N_2}$$

ii] Voltage ratio

$$E_1 = 4.44 \phi_m f N_1 \quad \text{--- (I)}$$

$$E_2 = 4.44 \phi_m f N_2 \quad \text{--- (II)}$$

Taking ratio (I) and (II)

$$\frac{E_1}{E_2} = \frac{4.44 \phi_m f N_1}{4.44 \phi_m f N_2}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

iii] equation for Voltage Ratio without load

$$\therefore V_1 = E_1$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\therefore \text{Voltage ratio} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

iv] transformation ratio (K)

$$\therefore K = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{V_2}{V_1}$$

v] Current ratio

$$\therefore V_1 I_1 = V_2 I_2$$

$$\therefore V_1 I_1 = V_2 I_2$$

$$\therefore \frac{V_1 I_1}{I_2} = \frac{V_2}{V_1}$$

using this equation


$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = K$$

Delta connection

Behaviour of a Pure resistance in Ac circuit.

→ R circuit
current i:-

Basic equation of I

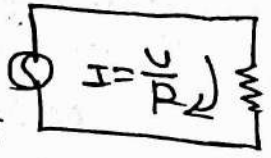

$$I = \frac{V}{R} \frac{V_m \sin \omega t}{R}$$

$$I = \left(\frac{V_m}{R}\right) \sin \omega t \text{ --- (1)}$$

standard equation of current is

$$I = I_m \sin (\omega t + \phi) \text{ --- (11)}$$

comparing (1) and (11)

$$I_m = \frac{V_m}{R} \text{ \& } \phi = 0$$

$$\therefore I = I_m \sin \omega t$$

Power:-

1) Instantaneous Power (P)

$$P = V \cdot I$$

$$V = V_m \sin \omega t \text{ and } I = I_m \sin \omega t$$

$$\therefore P = V_m \sin \omega t \text{ \& } I_m \sin \omega t.$$

$$P = V_m I_m \sin^2 \omega t \text{ --- (1)}$$

$$P = \frac{V_m I_m}{2} [1 - \cos (2\omega t)]$$

$$P = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos (2\omega t)$$

ii) Average Power (P_{av})

From equation No. 1

$$P_{av} = \frac{V_m I_m}{2}$$

$$P_{av} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \text{ --- } (\sqrt{2} \cdot \sqrt{2} = 2)$$

$$P_{av} = V_{rms} \cdot I_{rms} \text{ --- watt. t.}$$

Power:-

1) Active

$$S = V_{rms} [P = VI \cos \phi]$$


ii) Reactive

$$Q = VI \sin \phi$$

iii) Apparent


$$S = I_{rms} V_{rms}$$

Phasor:-

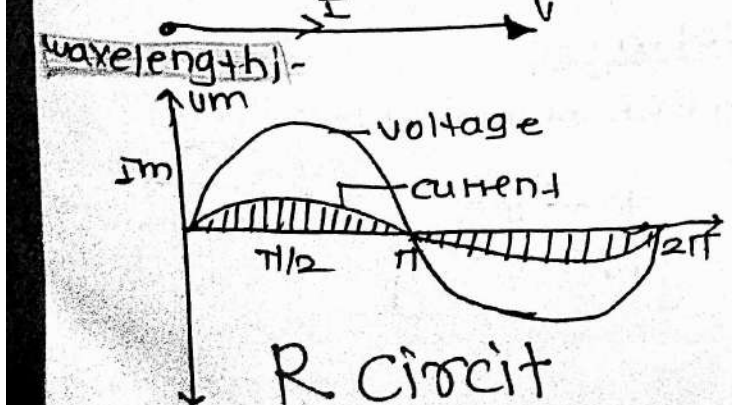

Behaviour of Pure inductor in Ac circuit

→ L circuit
current i:-

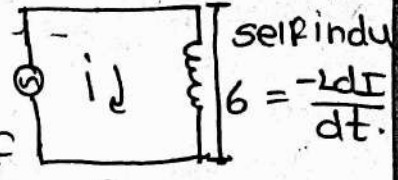

self induced emf

$$e = -L \frac{dI}{dt} \text{ supply of voltage is equal \& opposite}$$

$$\therefore V = -e = -(-L \frac{dI}{dt}) = L \frac{dI}{dt}$$

$$\text{Now } V = V_m \sin \omega t$$

$$\therefore V_m \sin \omega t$$

$$= L \frac{dI}{dt}$$

$$\therefore \frac{dI}{dt} = \frac{V_m \sin \omega t}{L}$$

$$\therefore dI = \frac{V_m}{L} \sin \omega t dt$$

By integration

$$I = \int dI = \int \frac{V_m}{L} \sin \omega t dt$$

use identity $\cos \omega t = \sin (\frac{\pi}{2} - \omega t)$

$$\therefore I = \frac{V_m}{\omega L} [\sin (\frac{\pi}{2} - \omega t)]$$

$$= \sin (\omega t - \frac{\pi}{2})$$

$$\therefore I = \frac{V_m}{\omega L} [\sin (\omega t - \frac{\pi}{2})]$$

$$\therefore I = I_m \sin (\omega t - \frac{\pi}{2})$$

Power:- $P = V \times I$

We have $V = V_m \sin \omega t$ \&

$$I = I_m \sin (\omega t - \frac{\pi}{2})$$

$$\therefore P = V_m I_m \sin (\omega t) \cdot \sin (\omega t - \frac{\pi}{2})$$

$$\therefore P = V_m I_m \frac{\sin (2\omega t)}{2}$$

$$\therefore P = \frac{V_m I_m}{2} - \sin (2\omega t)$$



- Active, Reactive Power

1) Active:- $Q = VI \sin \phi$

2) Reactive:- $P = VI \cos \phi$

3) Apparent:- $S = VI$

Phasor:-

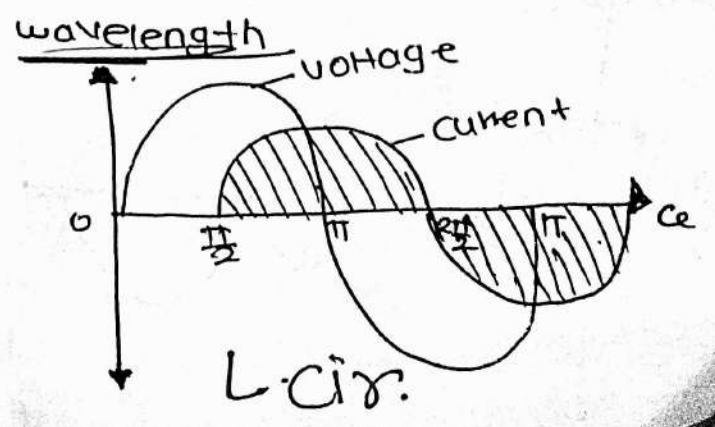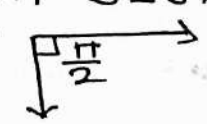

Behaviour like pure capacitor.

→ C-circuit
 $u = u_m \sin \omega t$
 current i :-

$$i = \frac{dq}{dt} = \frac{d}{dt} [u_m \sin \omega t]$$

$$= [u_m \frac{d}{dt} (\sin \omega t)]$$

$$\therefore i = (u_m \omega \cos \omega t) \quad \text{--- (1)}$$

Rearranging eqn no --- (1)

$$\therefore i = \frac{u_m}{\frac{1}{\omega C}} \cos \omega t$$

But $\cos \omega t = \sin(\omega t + \frac{\pi}{2})$

$$\therefore i = \frac{u_m}{\frac{1}{\omega C}} \sin(\omega t + \frac{\pi}{2})$$

$$\therefore i = I_m \sin(\omega t + \frac{\pi}{2})$$

derivation for I_m (where $\frac{u_m}{\frac{1}{\omega C}} = I_m$)
 Power.

$$P = U \times I$$

$$u = u_m \sin(\omega t) \text{ \& } I = I_m \sin \omega t$$

$$\therefore P = u_m \sin(\omega t) \cdot I_m \sin(\omega t + \frac{\pi}{2})$$

$$P = u_m I_m \sin(\omega t) \cdot \cos \omega t$$

where $\sin(\omega t + \frac{\pi}{2}) = \cos \omega t$

$$P = \frac{u_m I_m \sin(2\omega t)}{2}$$

$$P = \frac{u_m I_m}{2} \sin(2\omega t)$$


Active, reactive, apparent Power

1) Active :- $P = UI \cos \phi$


2) Reactive :- $Q = UI \sin \phi$

3) Apparent :- $S = U \times I$

Phasor diagram

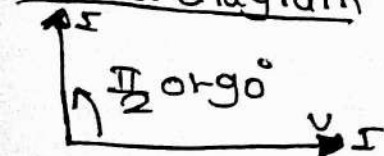

waveform

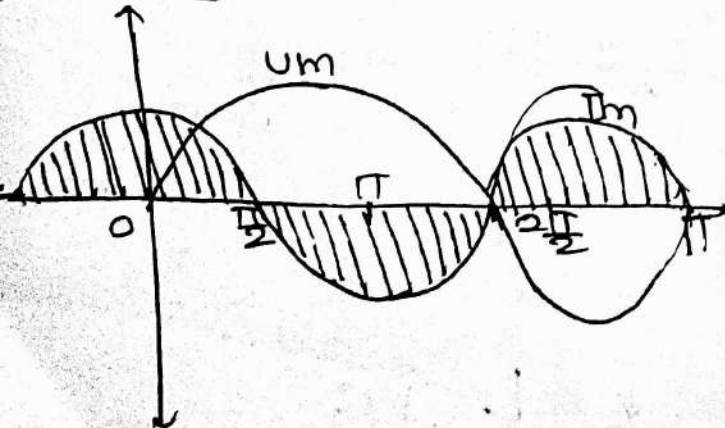

Series resonance:-
 consider the series R-L-C circuit as show in fig. (1)



$$u = u_m \sin \omega t$$

The impedance of circuit is given by

$$\therefore \bar{Z} = R + jX_L - jX_C$$

$$\bar{Z} = R + j\omega L - j\frac{1}{\omega C}$$

$$\bar{Z} = R + j\left[\omega L - \frac{1}{\omega C}\right]$$

At resonance $Z = R$ i.e. resistive

There fore the condition for

$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega_0^2 LC - 1 = 0$$

$$\omega_0^2 = \frac{1}{LC} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}}$$

$$P_0 = \frac{1}{2\pi\sqrt{LC}}$$

where

f_0 = Resonant Frequency of the CKT

Power factor :-

$$\therefore \cos \phi = \frac{P}{P_1} = 1$$

$$\cos \phi = 1$$

current :-

$$I_0 = \frac{U}{Z} = \frac{U}{R}$$


voltage :-

At Resonance $\omega_0 L = \frac{1}{\omega_0 C}$

$$\omega_0 L I_0 = \frac{1}{\omega_0 C} I_0$$

$$U_{L0} = U_{C0}$$

series R-L circuit.

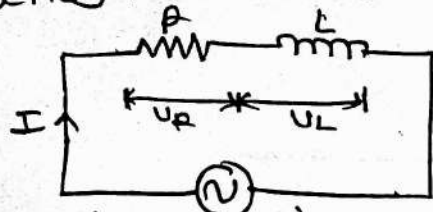


$$U_{rms} = U_m \sin \omega t.$$

Let, U_{rms} & I_{rms} - be the rms value of applied fig & current.

∴ Potential diff = $U_R = R \cdot I$ across R

∴ Potential diff = $U_L = X_L \cdot I$ across L

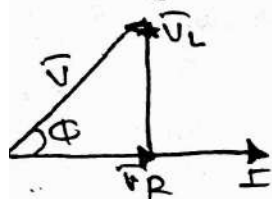∴ The U_R in phase with (I) whereas the U_L leads the current I by 90°



$$\cos \phi = \frac{U_R}{U}$$

Impedance:-

$$\bar{U} = \bar{U}_R + \bar{U}_L$$

$$= RI + jX_L I$$

$$\bar{U} = \bar{I} (R + jX_L)$$

$$\Rightarrow \boxed{\frac{\bar{U}}{\bar{I}} = R + jX_L = \bar{Z}}$$

$$\bar{Z} = Z \angle \phi \text{ — where } Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega^2 L^2}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

current:-

If the applied fig is given by

$$U = U_m \sin \omega t.$$


then the current eqn will be,

$$I = I_m \sin (\omega t - \phi)$$


$$\text{where } I_m = \frac{U_m}{Z}$$

$$\& \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

waveform:-

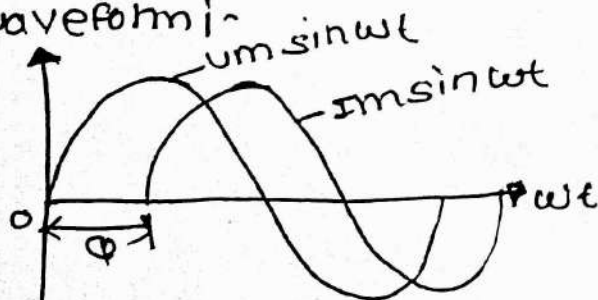

Phasor diagram:-

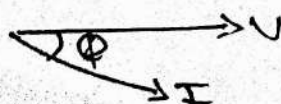

Power:-

① Instantaneous Power.

$$P = U \cdot I$$

$$= U_m \sin \omega t \cdot I_m \sin (\omega t - \phi)$$

$$= U_m I_m \sin \omega t \cdot \sin (\omega t - \phi)$$

$$P = U_m I_m \frac{1}{2} \{ \cos \phi - \cos (2\omega t - \phi) \}$$

$$\boxed{P = \frac{U_m I_m}{2} \cos \phi - \frac{U_m I_m}{2} \cos (2\omega t - \phi)}$$

② average Power.

$$P_{avg} = \frac{U_m I_m}{2} \cos \phi$$


$$P_{avg} = \frac{U_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$

$$\boxed{P_{avg} = U_{rms} I_{rms} \cos \phi} \quad (*)$$

Power triangle:-


In term of circuit-components

$$\cos \phi = \frac{R}{Z}$$

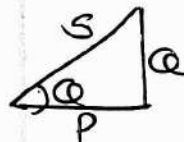

$$\boxed{\cos \phi = \frac{P}{S}}$$

series R-C circuit.

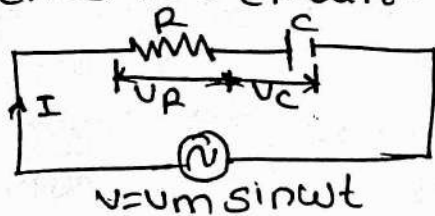

let V_{rms} & I_{rms} be the rms value of applied Vtg & I to a respectively.


∴ Potential diff = $V_R = RI$ across R

∴ Potential diff = $V_C = X_C I$ across C

∴ The voltage $\vec{V}$ is in phase with $\vec{I}$ where $\vec{V}_C$ lag behind the $(\vec{I})$ by 90° ∴ $\vec{V} = \vec{V}_R + \vec{V}_C$

Phasor diag:-

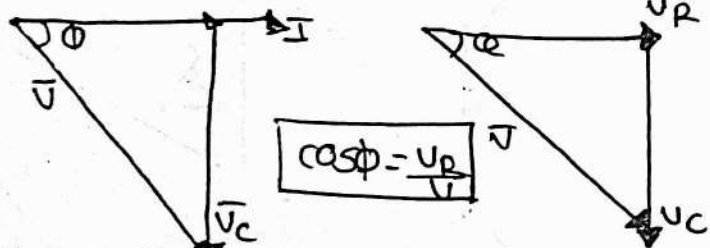The current $(\vec{I})$ flow through the R & C so, that $\vec{I}$ is take as the



Phasor diagram

voltage trian

Impedance:-

$$\vec{V} = \vec{V}_R + \vec{V}_C$$

$$= R\vec{I} - jX_C\vec{I}$$

$$\vec{V} = \vec{I}(R - jX_C)$$

$$\frac{\vec{V}}{\vec{I}} = R - jX_C = \vec{Z}$$

$$\therefore \vec{Z} = Z \angle -\phi$$


$$\therefore Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\text{and } \phi = \tan^{-1}\left(\frac{X_C}{R}\right)$$

$$\phi = \tan^{-1}\left(\frac{1}{\omega CR}\right)$$

where, $\vec{Z}$ is called complex impedance of series R-C

Impedance triangle

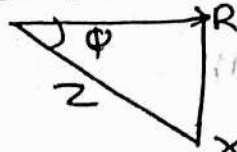

$$\cos \phi = \frac{R}{Z}$$

xc Impedance triangle

current:-


If the applied voltage is a given by $v = v_m \sin \omega t$.

$$I = I_m \sin(\omega t + \phi)$$

$$\text{where } I_m = \frac{V_m}{Z}$$

$$\therefore \phi = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{1}{\omega CR}\right)$$

waveform:-

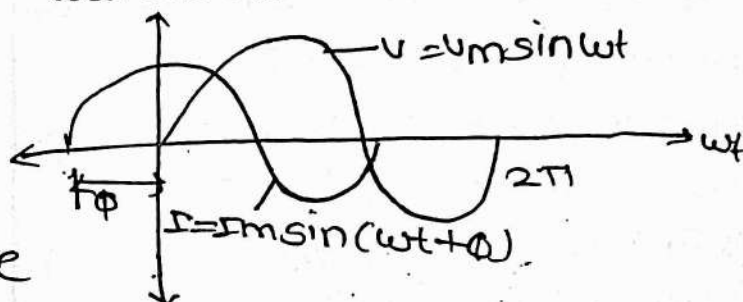

Power:-

$$\text{Active:- } VI \cos \phi = I^2 R$$

$$\text{Reactive:- } VI \sin \phi = I^2 X_C$$

$$\text{Apparent:- } VI = I^2 Z$$

Power triangle:-



Power factor:-


$$\text{voltage triangle } PF = \frac{V_R}{V}$$

$$\text{Impedance triangle } PF = \frac{R}{Z}$$

$$\text{Power triangle } PF = \frac{P}{S}$$

In case of an RC series ckt the power factor is leading in nature.

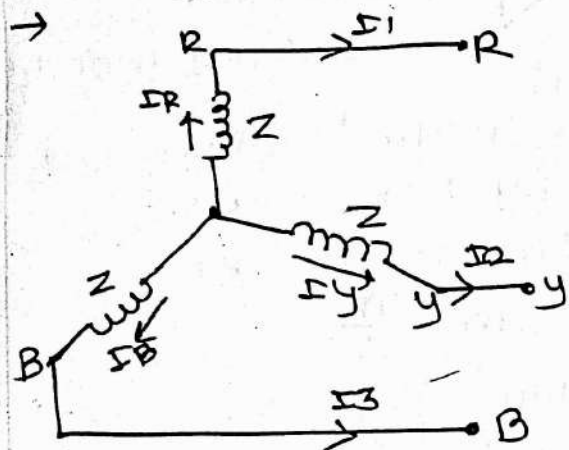Relation between line and phase value of current and voltage for balance 3-phase - **Star** connection



Line voltage - $V_L = V_{RY} = V_{YB} = V_{BR}$

Line current - $I_L = I_R = I_Y = I_B$

Phase voltage - $V_{ph} = V_{RY} = V_{YB} = V_{BR}$

Phase current - $I_{ph} = I_R = I_Y = I_B$

As path for line current I_L and Phase current I_{ph} is same

$$I_L = I_{ph}$$

$$\bar{V}_{RY} = \bar{V}_{RN} + \bar{V}_{NY}$$


$$\bar{V}_{NY} = -\bar{V}_{YN}$$

$$\bar{V}_{RY} = \bar{V}_{RN} - \bar{V}_{YN} \quad \text{--- (i)}$$

$$\bar{V}_{YB} = \bar{V}_{YN} - \bar{V}_{BN} \quad \text{--- (ii)}$$

$$\bar{V}_{BY} = \bar{V}_{BN} - \bar{V}_{RN} \quad \text{--- (iii)}$$

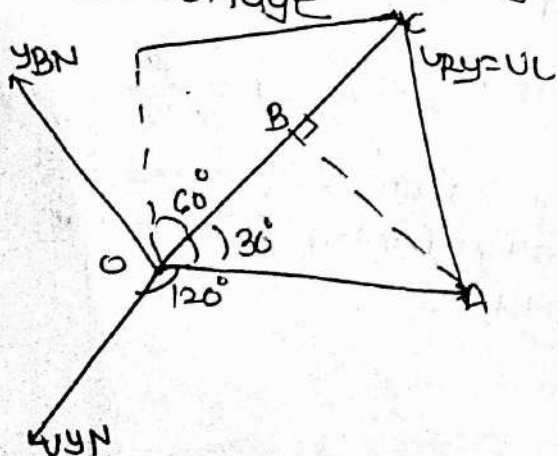The phase diagram will give a relation betⁿ line voltage and phase voltage



Phasor diagram for the resistive load.

Angle betⁿ V_{RN} & $-V_{YN}$ is 60°
So $\angle AOB = 30^\circ$


from ΔAOB $\cos 30^\circ = \frac{OB}{OA} = \frac{V_{ph}}{V_L}$

$$\frac{\sqrt{3}}{2} = \frac{V_{ph}}{V_L}$$


$$V_L = \sqrt{3} V_{ph}$$

Thus line voltage is $\sqrt{3}$ times the phase voltage & line current & phase current are same.

Phasor dia for Inductive load

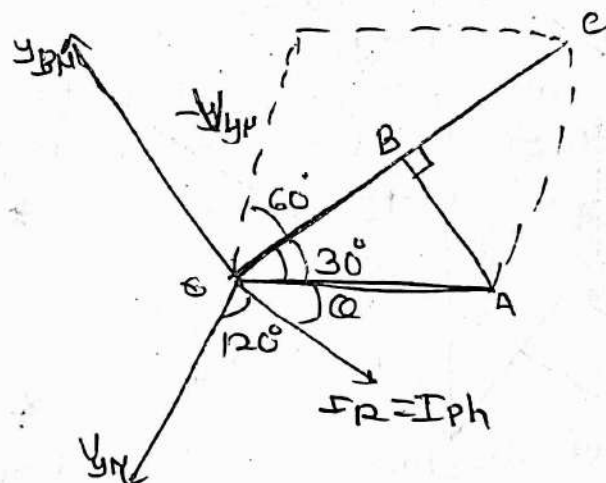

Phasor dia. for capacitive load

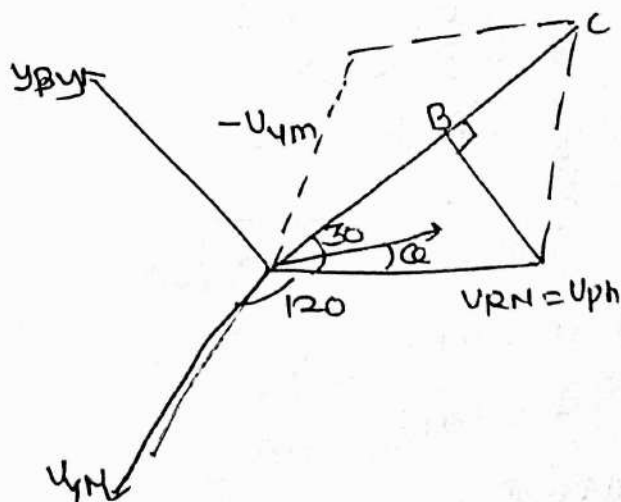

① Work Power energy

[with usual notation derive the expression, $a_2 = \frac{a_1}{(1 + a_1(t_2 - t_1))}$]

→ Let us consider a conducting material whose initial resistance is R_1 at temperature $t_1^\circ\text{C}$ i.e. at Point A.

The expression for R_2 ,

$$R_2 = R_1 [1 + a_1 \cdot (t_2 - t_1)] \quad \text{--- (I)}$$

where a_1 is T.C.R at $t_1^\circ\text{C}$

The expression for R_1

$$R_1 = R_2 [1 + a_2 \cdot (t_1 - t_2)] \quad \text{--- (II)}$$

where a_2 is T.C.R at $t_2^\circ\text{C}$

From eqn (I) & (II) taking ratio

$$\frac{R_1}{R_2} = 1 + a_2(t_2 - t_1) \quad \text{--- (III)}$$

$$= \frac{1}{1 + a_1(t_2 - t_1)} \quad \text{--- (IV)}$$

From equation (III) & (IV)

$$\begin{aligned} a_2(t_2 - t_1) &= \frac{1}{1 + a_1(t_2 - t_1)} - 1 \\ &= \frac{1 - 1 + a_1(t_2 - t_1)}{1 + a_1(t_2 - t_1)} = \frac{-a_1(t_2 - t_1)}{1 + a_1(t_2 - t_1)} \end{aligned}$$

multiplying both side

$$a_2(t_2 - t_1) = \frac{a_1(t_2 - t_1)}{1 + a_1(t_2 - t_1)}$$

$$a_2 = \frac{a_1}{1 + a_1(t_2 - t_1)} \quad \text{--- (V)}$$


If we consider

$$a_1 = \frac{a_0}{1 + a_0 t}$$

from equation (V)

$$a_1 - a_2 = a_1 a_2 (t_2 - t_1)$$

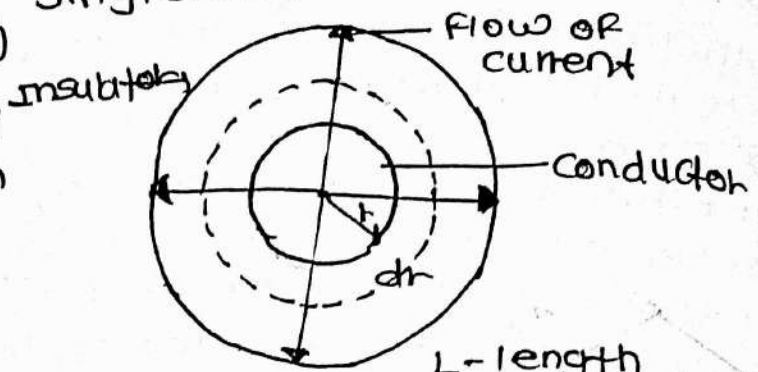2) derive the expression for the insulation resistance of the single core cable.



$$R = \frac{\rho L}{a} \quad \text{--- (I)}$$

L - length
 ρ - Resistivity
 R - Resistance
 a - cross area

$$dR_i = \frac{\rho dr}{2\pi r L}$$

$$\therefore R_i = \int_{R_1}^{R_2} dR_i \quad \text{--- (II)}$$

Put equation in (I) & (II)

$$\therefore R_i = \int_{R_1}^{R_2} \frac{\rho dr}{2\pi r L}$$

$$R_i = \frac{\rho}{2\pi L} \int_{R_1}^{R_2} \frac{dr}{r}$$

$$R_i = \frac{\rho}{2\pi L} [\log r]_{R_1}^{R_2}$$

$$R_i = [\log e R_2 - \log e R_1]$$

where $\log e = 2.303$

$$R_i = [\log e R_2 - \log e R_1]$$

$$R_i = \frac{\rho}{2\pi L} \log e \left[\frac{R_2}{R_1} \right]$$

where:-

ρ = density

L = length

R_1 = radius of conductor

R_2 = radius of conductor + insulation

3) derive the expression for the conversion of a delta connected into an equivalent star circuit
→



Resistance betⁿ terminal 1 & 2
for delta: $= \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (1)}$

for star: $= R_1 + R_2 \quad \text{--- (2)}$

equating (1) and (2)

$$\frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} = R_1 + R_2 \quad \text{--- (3)}$$

Similarly for resistance 3 and 1

$$\frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} = R_1 + R_3 \quad \text{--- (4)}$$

Also for resistance 2 and 3

$$\frac{R_{23}(R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} = R_2 + R_3 \quad \text{--- (5)}$$

let find R_1, R_2, R_3 in term of R_{12}, R_{23}, R_{31}

R_{31} sub eqⁿ (4) & (5)

$$\frac{R_{23}(R_{31} + R_{12}) - R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} = R_2 - R_1 \quad \text{--- (6)}$$

Add eqⁿ (3) & (6)


$$\therefore \frac{2R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} = 2R_2$$

$$\therefore R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$\text{Similarly, } R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\text{and } R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

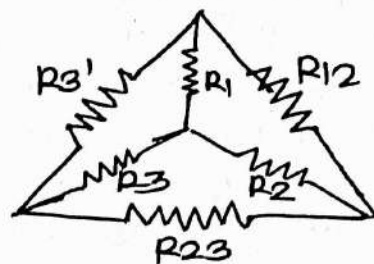4) derive the expression for the conversion of star connected in an delta connect
→



The resistance betⁿ terminals R_1, R_2 & R_3

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (I)}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (II)}$$

$$R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (III)}$$

multiply eqⁿ (I) & (II)

$$R_1 \cdot R_2 = \frac{R_{12}(R_{23} \cdot R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (IV)}$$

$$R_2 \cdot R_3 = \frac{R_{23}(R_{12} \cdot R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (V)}$$

$$R_1 \cdot R_3 = \frac{R_{31}(R_{12} \cdot R_{23})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (VI)}$$

Add eqⁿ (4) (5) & (6)

$$\begin{aligned} & R_1 R_2 + R_2 R_3 + R_1 R_3 \\ &= \frac{(R_{12}^2 R_{23} R_{31} + R_{23}^2 R_{12} R_{23} R_{31} + R_{31}^2 R_{12} R_{23} R_{31})}{[R_{12} + R_{23} + R_{31}]} \end{aligned}$$

Taking common

$$= \frac{R_{12} R_{23} R_{31}}{[R_{12} + R_{23} + R_{31}]}$$

$$R_1 R_2 + R_2 R_3 = R_1 R_{23}$$

$$R_{23} = \frac{R_2 + R_3 + R_1}{R_1}$$

$$\left[R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \right] \text{ similarly}$$



$$\left[R_2 = R_1 + R_2 + \frac{R_1 R_2}{R_3} \right]$$

$$\left[R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} \right]$$

derive the theorem for the a Superposition theorem.

Statement 1:- In any linear bilateral network in the connecting two or more energy source on the voltage across an a current through any element is an the algebraic summation of the voltage or current to produced by on the individual source on to acting alone.

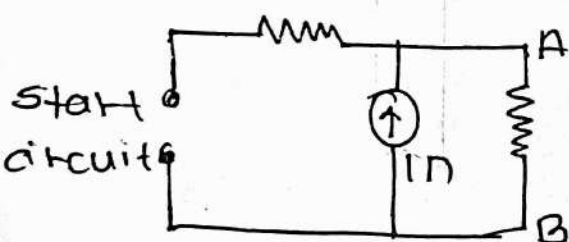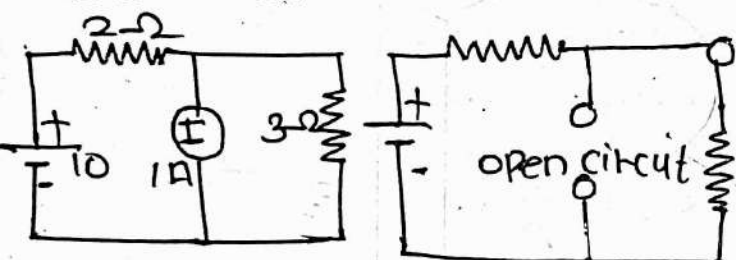- while the source are two o replaced by their internal resistance.



$$R_T = 2 + 3 = 5\Omega$$

$$\text{current } (I') = \frac{\text{Total voltage}}{\text{Total resistance}}$$

$$I' = \frac{10}{5}$$

$$I' = 2A \downarrow$$

Formula 1:-

current in any branch

$$= \frac{\text{supply current} \times \text{open branch}}{\text{Addition of resistance}}$$

$$I'' = \frac{1 \times 2}{2 + 3}$$

$$= \frac{2}{5}$$

$$I'' = 0.4A \downarrow$$


Kirchhoff current law (KCL)
Statement 1:- Algebraic sum of the current meeting at any the junction point in an electric circuit is always zero

$$\sum I = 0$$

In other word at any junction or node is an electric the circuit, sum of incoming a current is equal to sum of outgoing current.

$$\text{ie any node } \sum I_C = \sum O_C$$

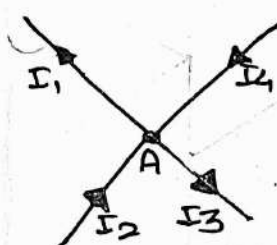Explanation 1:- consider a node as show in fig



four branch meet at junction or node

$$I_2 + I_4 = I_1 + I_3$$

Kirchhoff voltage law (KVL)

Statement 1:- In any electrical network, algebraic sum of V drop across various element around any closed loop


$$\sum IR = \sum E$$

In other word, if we trace any closed path or loop in an electrical network an algebraic sum of branch voltage is always zero

$$\sum V = 0$$

Explanation 1:-

consider a network show below

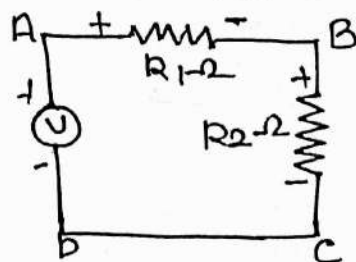

using KVL

$$\sum V = 0$$

$$-IR_1 - IR_2 + V = 0 \quad V = I(R_1 + R_2)$$

$$I = (V / (R_1 + R_2))$$